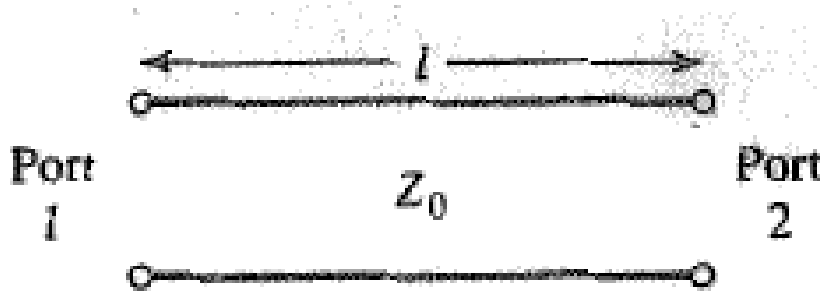


EE6311 Fall 2009, Design Project #1, Impedance Matching

1. Derive the scattering matrix for the lossless transmission line shown below, relative to a system impedance of Z_0 . Verify that the matrix satisfies the unitary condition. (Given during streaming lecture on 9/28)



2. (a) Using ideal lumped-element components, design a 2-element matching network to match a $100\text{-}\Omega$ source (port 1) to a load impedance, $Z_L = 50 + j15\ \Omega$ at 10 GHz. Obtain two solutions. (Given during streaming lecture on 9/30).

(b) Convert to the appropriate L and C values at 10 GHz **simulate** your results. This will be a 1-port circuit where you change your load impedance from $50\ \Omega$ to $50 + j15\ \Omega$ and include ideal L and C values for the matching networks. Plot the magnitude of S_{11} (in dB) from 8 to 12 GHz.

3. Design a single-section quarter-wave matching transformer to match a $250\ \Omega$ load to a $50\ \Omega$ line. What is the percent bandwidth of this transformer, for SWR less than or equal to ≤ 1.5 . If the design frequency is 6 GHz, what are the dimensions of the microstrip lines and matching network. Assume the substrate is 0.159 cm thick, with a dielectric constant of 2. No need to simulate, just include dimensions.

4. Design a microstrip impedance matching network using a single shunt-stub tuner with an open- or short-circuited stub to match $75\ \Omega$ to a load impedance of $100 + j80\ \Omega$. **Simulate** your results and plot the magnitude of S_{11} in dB over the frequency range of 8 to 12 GHz.

Use center frequency $f_0 = 10\ \text{GHz}$

Port impedances = $50\ \Omega$

Substrate $\epsilon_r = 12$

Substrate thickness = 0.381 mm

Conductor thickness = Au metal at $10\ \mu\text{m}$